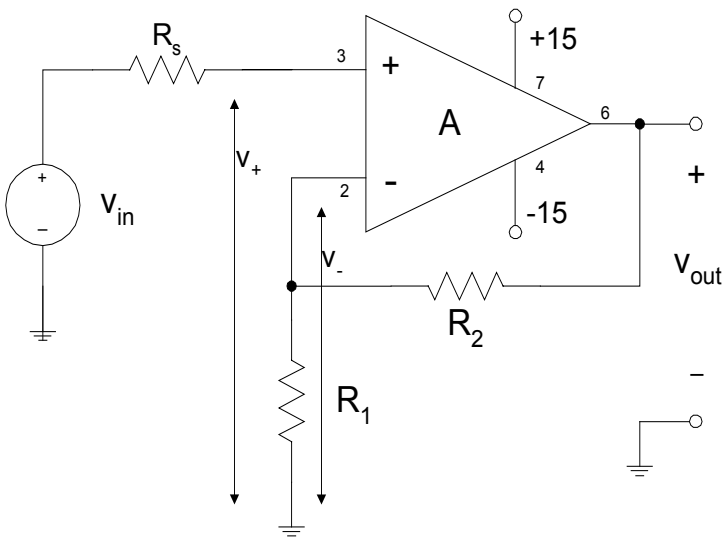


## NON-INVERTING AMPLIFIER GAIN ANALYSIS using FINITE OPEN LOOP GAIN examples

Refer to Figure 7 of the Motorola MC 1741C spec: Open-Loop Frequency Response



Let  $R_s = 0$ ; Therefore  $v_+ = v_{in}$

$$v_- = \frac{R_1}{R_1 + R_2} \times v_{out}; \quad \text{but } v_+ = v_-$$

$$\text{so } v_{in} = \frac{R_1}{R_1 + R_2} \times v_{out};$$

$$\frac{v_{out}}{v_{in}} = \frac{R_1 + R_2}{R_1}$$

$$\text{or } A_v = 1 + \frac{R_2}{R_1}$$

### FINITE OPEN-LOOP GAIN ANALYSIS: Examples at 1 Hz, 1000 Hz, and 10kHz

Voltage gain  $A_v = 40\text{dB} = 100$ ;  $R_2 = 100\text{k}\Omega$ ,  $R_1 = 1\text{k}\Omega$ ; [OK  $101 = 40.1\text{dB}$ !]

- At 1 Hz,  $A_{vol} = 100\text{ dB} = 1 \times 10^5 = 100,000$ .

$$A_v = \frac{A}{1 + A\beta} = \frac{10^5}{1 + 10^5 \times .01} = \frac{10^5}{10^3} = 100 = 40\text{ dB}$$

Note:  $A\beta = 10^3 = 60\text{ dB}$ ;  $60\text{ dB}$  loop gain +  $40\text{ dB}$  closed loop gain =  $100\text{ dB}$  total gain

- At 1000 Hz,  $A_{vol} = 60\text{ dB} = 10^3 = 1000$ .

$$A_v = \frac{A}{1 + A\beta} = \frac{10^3}{1 + 10^3 \times .01} = \frac{10^3}{1 + 10} = \frac{1000}{11} = 90.9 = 39.2\text{ dB}$$

Note:  $A\beta = 10^1 = 20\text{ dB}$ ;  $20\text{ dB}$  loop gain +  $40\text{ dB}$  closed loop gain =  $60\text{ dB}$  total gain

- At 10 kHz,  $A_{vol} = 42\text{ dB} = 1.26 \times 10^2 = 126$ .

$$A_v = \frac{A}{1 + A\beta} = \frac{126}{1 + 126 \times .01} = \frac{126}{1 + 1.26} = \frac{126}{2.26} = 55.8 = 34.9\text{ dB}$$

Note:  $A\beta = 1.26 = 2.0\text{ dB}$ ;  $2\text{ dB}$  loop gain +  $40\text{ dB}$  closed loop gain =  $42\text{ dB}$  total gain