

MASSACHUSETTS INSTITUTE OF TECHNOLOGY

Department of Electrical Engineering and Computer Staff

6.301 Solid State Circuits

Spring Term 2003  
Problem Set 5


Issued : March 14, 2003  
Due : Friday, March 21, 2003

---


**Problem 1:** Current Mirrors.

- (a) For each of the following current mirrors, express  $I_{out}/I_{in}$  as a fraction of expanded polynomials in  $\beta$ . Also, solve for the lower bound of  $V_{OUT}$  such that all transistors remain Forward Active in terms of  $V_{BE}$  and  $V_{CE,sat}$ . You cannot neglect base currents.


- (i) Improved Current Mirror:

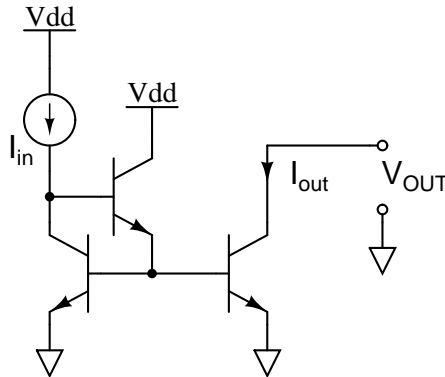

- (ii) Cascode Current Mirror:

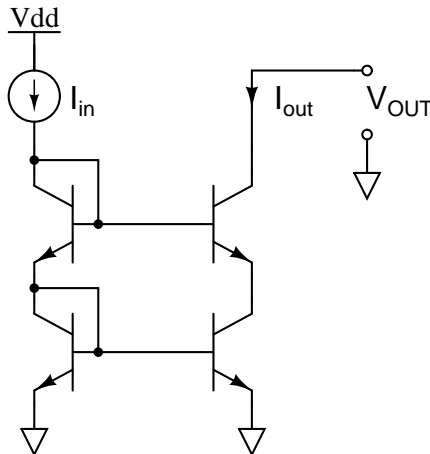


(iii) Improved Wilson Current Mirror:

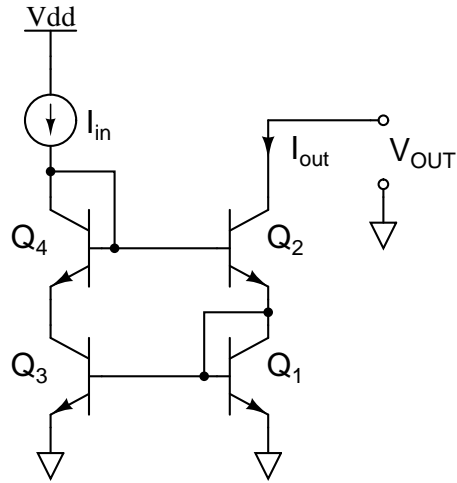


(b) Calculate  $R_o$  for the Improved Wilson Current Mirror. First, write it in terms of small-signal parameters  $r_o$ ,  $g_m$  and  $r_\pi$ ; then make some approximations to simplify your expression.

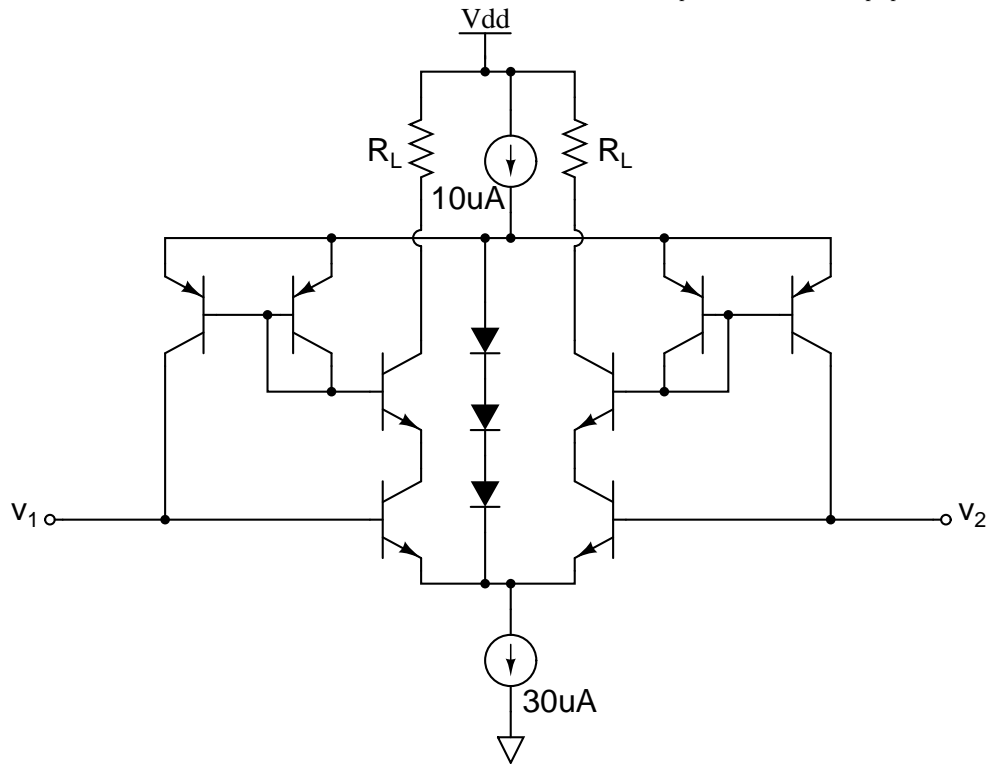**Problem 2:** The following is a simplified version of the input stage for the OP07 Ultralow Offset Voltage Operation Amplifier from Analog Devices. Calculate the input current flowing into  $v_1$  for common-mode inputs assuming  $\beta_{npn}=200$  and  $\beta_{pnp}=40$ .




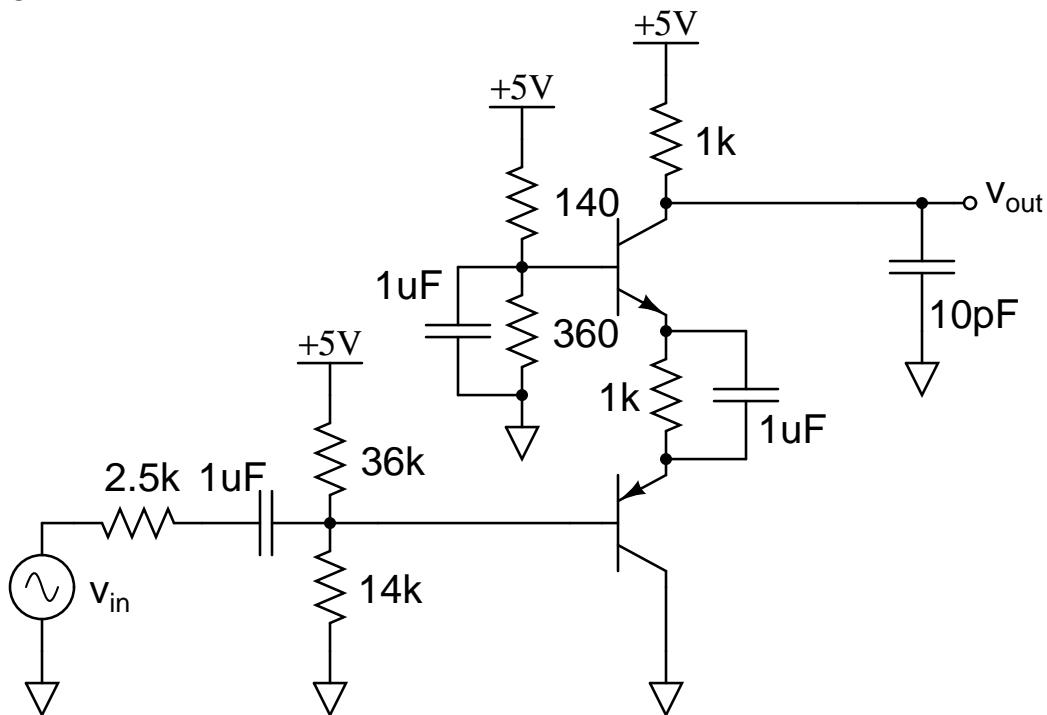**Problem 3:** The following amplifier is in a stacked Emitter-Follower, Common-Base configuration. Assume  $V_{BE,on}=0.6V$ ,  $c_{\mu}=2pF$ ,  $c_{\pi}=20pF$ ,  $\beta_{npn}=200$  and  $\beta_{ppn}=100$ . You may neglect  $r_b$  and  $r_o$ .




- Calculate the midband small-signal gain.
- Using the OCT method, estimate the upper  $-3dB$  frequency.
- Using the SCT method, estimate the lower  $-3dB$  frequency.

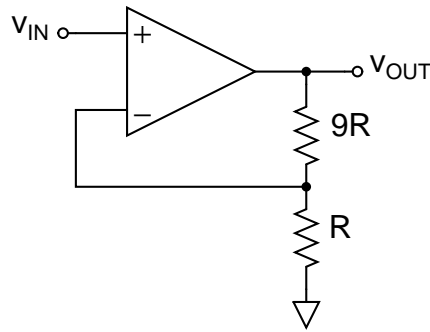**Problem 4:** Operational Amplifiers. Consider the following non-inverting configuration:



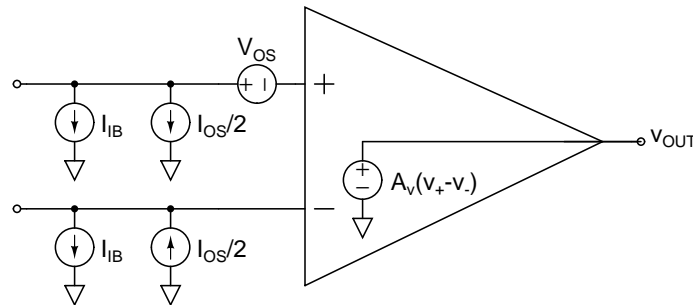We know that practical op amp circuits do not implement “ideal op amp” behavior. This is the op amp equivalent circuit including Input Offset Voltage  $V_{OS}$ , Input Bias Current  $I_{IB}$ , Input Offset Current  $I_{OS}$ , and Finite Gain  $A_V$ :



- (a) For the non-inverting op amp configuration, solve  $v_{OUT}$  in terms of  $v_{IN}$  and the following non-idealities.
- (i) Input Offset Voltage  $V_{OS}$  (assuming no  $I_{IB}$  or  $I_{OS}$ ; and infinite gain)
  - (ii) Input Bias Current  $I_{IB}$  (assuming no  $V_{OS}$  or  $I_{OS}$ ; and infinite gain)
  - (iii) Input Offset Current  $I_{OS}$  (assuming no  $V_{OS}$  or  $I_{IB}$ ; and infinite gain)
  - (iv) Finite Gain  $A_V$  (assuming no  $V_{OS}$ ,  $I_{IB}$  or  $I_{OS}$ )
- (b) It is possible to counteract the dependence on  $I_{IB}$  found in part (a-ii) with a resistor in series with the non-inverting terminal. Find the value of  $R'$  which eliminates the dependence on  $I_{IB}$  found in part (a-ii).

